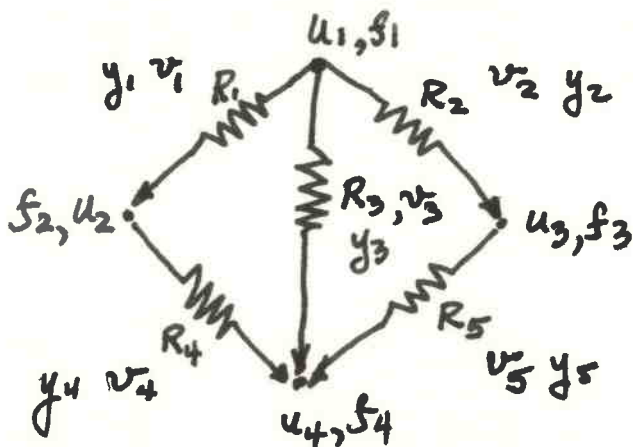


Math 415 Lecture 26

Sec 6.2 Electrical Networks (in equilibrium)



u_i 's are the voltage potentials at each node

R_i 's are the resistances of the wires

The voltage v_i in each wire is the difference in voltage potentials

$$\begin{aligned} v_1 &= u_1 - u_2 \\ v_2 &= u_1 - u_3 \\ v_3 &= u_1 - u_4 \\ v_4 &= u_2 - u_4 \\ v_5 &= u_3 - u_4 \end{aligned}$$

Let y_i denote the current in the i th wire but f_i denote the external current entering each node.

Write in matrix form

$$v = Au$$

$$A = \begin{pmatrix} 1 & -1 & 0 & 0 \\ 1 & 0 & -1 & 0 \\ 1 & 0 & 0 & -1 \\ 0 & 1 & 0 & -1 \\ 0 & 0 & 1 & -1 \end{pmatrix}$$

= incident matrix of the network

We need to interconnect y, v, R_i 's and u_i 's.

Kirchhoff's Law of Voltage The sum of the ~~currents~~ voltages around each closed circuit is zero

$$\begin{aligned} v_1 + v_4 - v_3 &= 0, & v_2 + v_5 - v_3 &= 0 \\ \text{ie } (1 \ 0 \ -1 \ 1 \ 0) \cdot v &= 0, & (0 \ 1 \ -1 \ 0 \ 1) \cdot v &= 0 \end{aligned}$$

Question: Given a set of voltages v_i in the wires, can

we find the corresponding voltage potentials?
 For this to be the case we need $v \in \text{rng } A$. By
 Fredholm's criterion this is true iff v is orthogonal to
 $\text{coker } A$. But these are the circuits, so Kirchhoff's Voltage
 Law ensures this! (Topology of the Network)

Ohm's Law (What is the constitutive content of Network)
 ($V = RI$ - for a fixed voltage, there is more current
 in lower resistance wires)

Here $v_k = R_k y_k$

or $v = R y$

or $y = C v$

Resistance Matrix

$R = \text{diag}(R_1, \dots, R_5)$

$C = \text{diag}(C_1, \dots, C_5)$

$= \text{diag}(\frac{1}{R_1}, \dots, \frac{1}{R_5})$

= conductance matrix.

Kirchhoff's Current Law The net current leaving a
 node equals the external current coming into a node.

Example: If a 1 amp current is sent into node 1
 and no other external currents, then $f_1 = 1, f_2 = f_3 = f_4 = 0$

So $y_1 + y_2 + y_3 = 1, -y_1 + y_4 = 0, -y_2 + y_5 = 0, -y_3 - y_4 - y_5 = 0$

$(1 \ 1 \ 1 \ 0 \ 0) \cdot y = 1, (-1 \ 0 \ 0 \ 1 \ 0) \cdot y = 0$

$(0 \ -1 \ 0 \ 0 \ 1) \cdot y = 0, (0 \ 0 \ -1 \ -1 \ -1) \cdot y = 0$

ie $A^T y = f$

So we have $v = Au$, $y = Cv$, $f = A^T y$
 or $Ku = f$ where $K = A^T C A =$ resistivity matrix of the network! ← Gram Matrix!

In our case

$$K = \begin{pmatrix} c_1 + c_2 + c_3 & -c_1 & -c_2 & -c_3 \\ -c_1 & c_1 + c_4 & 0 & -c_4 \\ -c_2 & 0 & c_2 + c_5 & -c_5 \\ -c_3 & -c_4 & -c_5 & c_3 + c_4 + c_5 \end{pmatrix}$$

If $R_i = 1$ for all i , then

$$Ku = f \text{ becomes } \begin{pmatrix} 3 & -1 & -1 & -1 \\ -1 & 2 & 0 & -1 \\ -1 & 0 & 2 & -1 \\ -1 & -1 & -1 & 3 \end{pmatrix} u = \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

$$(K | f) \rightarrow (\text{Gaussian Elim}) \rightarrow \left(\begin{array}{cccc|c} 3 & -1 & -1 & -1 & 1 \\ 0 & 5/3 & -1/3 & -4/3 & 1/3 \\ 0 & 0 & 8/3 & -8/3 & 2/3 \\ 0 & 0 & 0 & 0 & 1 \end{array} \right)$$

Wow! Explain in terms of "excess current cannot lead to equilibrium".

So what f 's are acceptable? K is singular! Why? Relate to fact that $\ker A$ has dimension 1.

$\ker A = \text{span} \left\{ \begin{pmatrix} 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} \right\}$. Thus $\ker K = \text{span} \left\{ \begin{pmatrix} 1 \\ 1 \\ 1 \\ 1 \end{pmatrix} \right\}$
 Hence f must be \perp to $\text{coker } K$, i.e. $\perp \text{coker } K$ (since K is sym)
 $(1 \dots 1) \cdot f = 0$ or $f_1 + \dots + f_5 = 0$ Makes sense!

Example Suppose $k_i = 1 \forall i$ and $f = \begin{pmatrix} 1 \\ 0 \\ 0 \\ -1 \end{pmatrix}$.

Then by Gaussian Elimination we find that

$$u = \begin{pmatrix} \frac{1}{2} + t \\ \frac{1}{4} + t \\ \frac{1}{4} + t \\ t \end{pmatrix} = \begin{pmatrix} \frac{1}{2} \\ \frac{1}{4} \\ \frac{1}{4} \\ 0 \end{pmatrix} + t \begin{pmatrix} 1 \\ 1 \\ 1 \\ 1 \end{pmatrix}$$

is this expected?

How can we eliminate the ambiguity?

Minimum norm sol'n is one possibility.

Here we consider, instead, "grounding" one node, i.e. $u_i = 0$ for some i . If we choose $u_4 = 0$, the above shows that $t = 0$ so the other u_i 's are determined.

But we could find this via a reduced problem. Eliminate the i^{th} column from A and the i^{th} row and column from K and i^{th} entry of f .